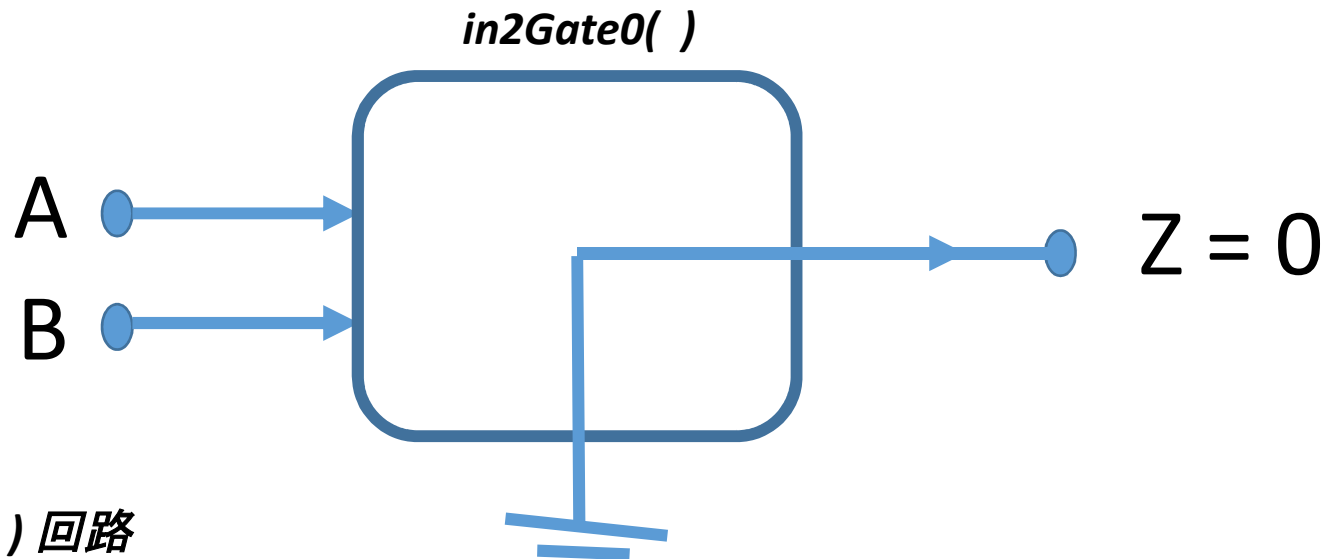


2入力1出力論理ゲート *in2Gate0()*回路の動作説明



in2Gate0() 回路


A	B	Z
0	0	0
0	1	0
1	0	0
1	1	0

DCDL Code for *in2Gate0()* 回路

```
define in2Gate0( ) { input A, B; output Z;  
  
                    Z = 0; }
```

$$(0)_{10} = (0000)_2 = (0)_{16}$$

2入力1出力論理ゲート *in2Gate1()*回路の動作説明

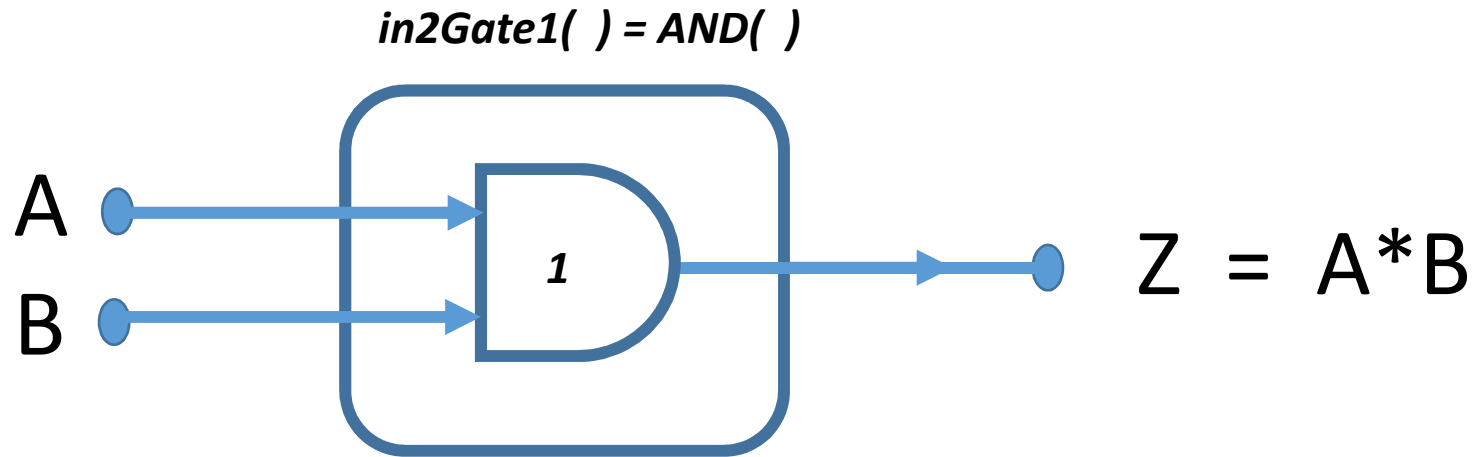

in2Gate1() 回路


A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

DCDL Code for *in2Gate1()* 回路

```
define in2Gate1( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = A * B ; }
```

$$(1)_{10} = (0001)_2 = (1)_{16}$$

2入力1出力論理ゲート *in2Gate2()*回路の動作説明

 

in2Gate2() 回路


A	B	Z
0	0	0
0	1	0
1	0	1
1	1	0

DCDL Code for *in2Gate2()* 回路

```
define in2Gate2( ) { input A, B; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ= A*(1 - B) ; }
```

$$(2)_{10} = (0010)_2 = (2)_{16}$$

2入力1出力論理ゲート *in2Gate3()*回路の動作説明

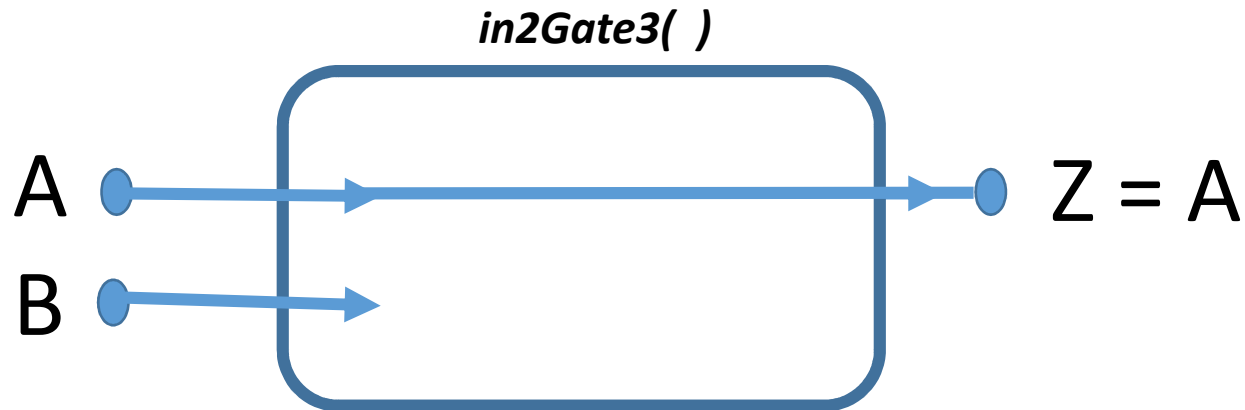

in2Gate3() 回路


A	B	Z
0	0	0
0	1	0
1	0	1
1	1	1

DCDL Code for *in2Gate3()* 回路

```
define in2Gate3( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;    ZZ = A ; }
```

$$(3)_{10} = (0011)_2 = (3)_{16}$$

2入力1出力論理ゲート *in2Gate4()*回路の動作説明

 

in2Gate4() 回路


A	B	Z
0	0	0
0	1	1
1	0	0
1	1	0

DCDL Code for *in2Gate4()* 回路

```
define in2Gate4( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = (1 - A) * B ; }
```

$$(4)_{10} = (0100)_2 = (4)_{16}$$

2入力1出力論理ゲート *in2Gate5()*回路の動作説明

 

in2Gate5() 回路

A	B	Z
0	0	0
0	1	1
1	0	0
1	1	1


DCDL Code for *in2Gate5()* 回路

```
define in2Gate5( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = B ; }
```

$$(5)_{10} = (0101)_2 = (5)_{16}$$

2入力1出力論理ゲート in2Gate6()回路の動作説明

in2Gate6()=EXOR()

 

in2Gate6()回路


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

DCDL Code for in2Gate6()回路

```
define in2Gate6( ) { input A, B ; output Z ;
    memory ZZ ;
    Z = ZZ ;
    ZZ=( 1 - A ) *B + A*(1 - B) ; }
```

$$(6)_{10} = (0110)_2 = (6)_{16}$$

2入力1出力論理ゲート *in2Gate7()*回路の動作説明

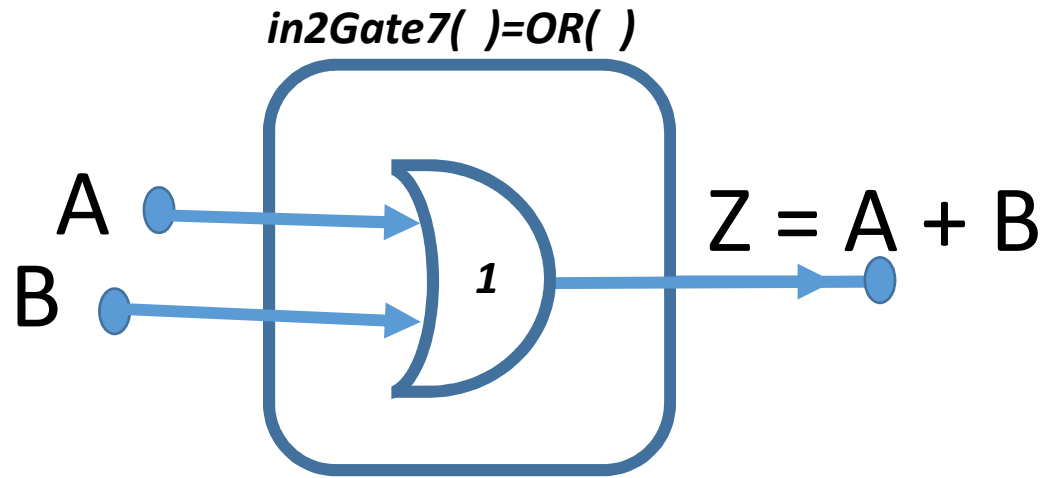

in2Gate7() 回路


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

DCDL Code for *in2Gate7()* 回路

```
define in2Gate7( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = A + B - A*B ; }
```

$$(7)_{10} = (0111)_2 = (7)_{16}$$

2入力1出力論理ゲート *in2Gate8()*回路の動作説明

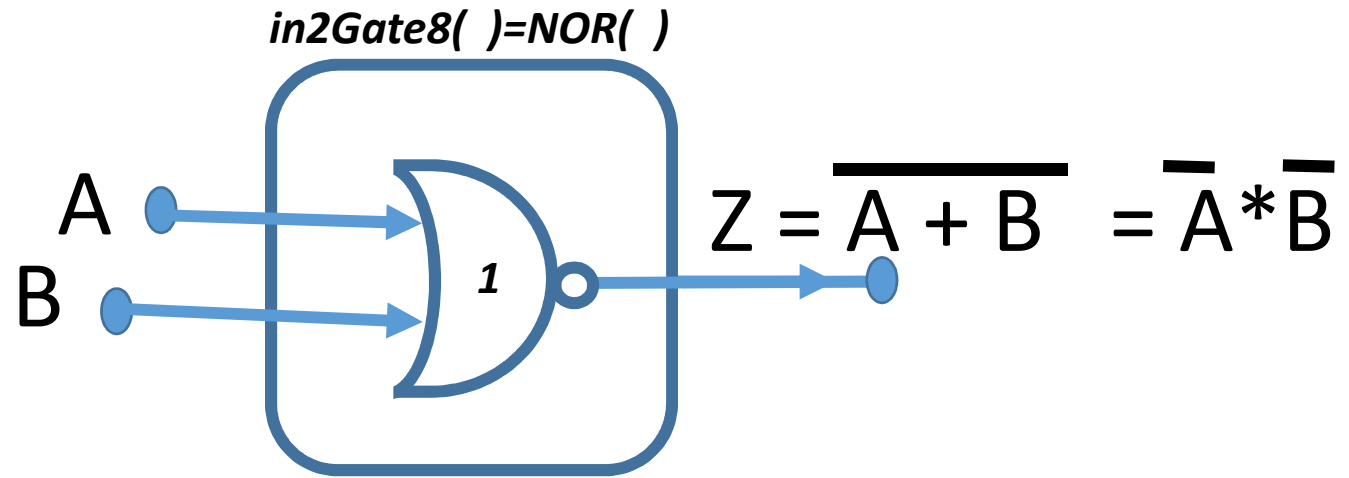

in2Gate8() 回路

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0


DCDL Code for *in2Gate8()* 回路

```
define in2Gate8( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = (1 - A) * (1 - B) ; }
```

$$(8)_{10} = (1000)_2 = (8)_{16}$$

2入力1出力論理ゲート *in2Gate9()*回路の動作説明

in2Gate9() = EXNOR()

 

in2Gate9() 回路


A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

DCDL Code for *in2Gate9()* 回路

```
define in2Gate9( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = A*B + ( 1 - A)*(1 - B) ; }
```

$$(9)_{10} = (1001)_2 = (9)_{16}$$

2入力1出力論理ゲート *in2GateA()*回路の動作説明

 

in2GateA() 回路


A	B	Z
0	0	1
0	1	0
1	0	1
1	1	0

DCDL Code for *in2GateA()* 回路

```
define in2GateA( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = 1 - B ; }
```

$$(10)_{10} = (1010)_2 = (A)_{16}$$

2入力1出力論理ゲート in2GateB()回路の動作説明

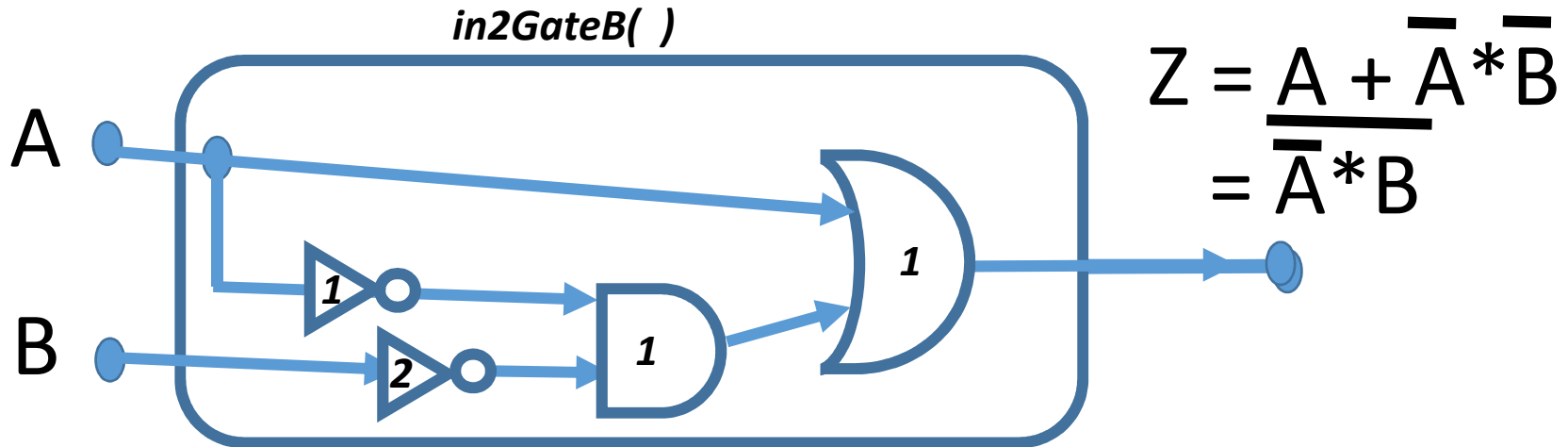

in2GateB() 回路


A	B	Z
0	0	1
0	1	0
1	0	1
1	1	1

DCDL Code for in2GateB() 回路

```
define in2GateB( ) { input A, B ; output Z ;
    memory ZZ ;
    Z = ZZ ;
    ZZ = A + (1 - A) * (1 - B) ; }
```

$$(11)_{10} = (1011)_2 = (B)_{16}$$

2入力1出力論理ゲート in2GateC()回路の動作説明

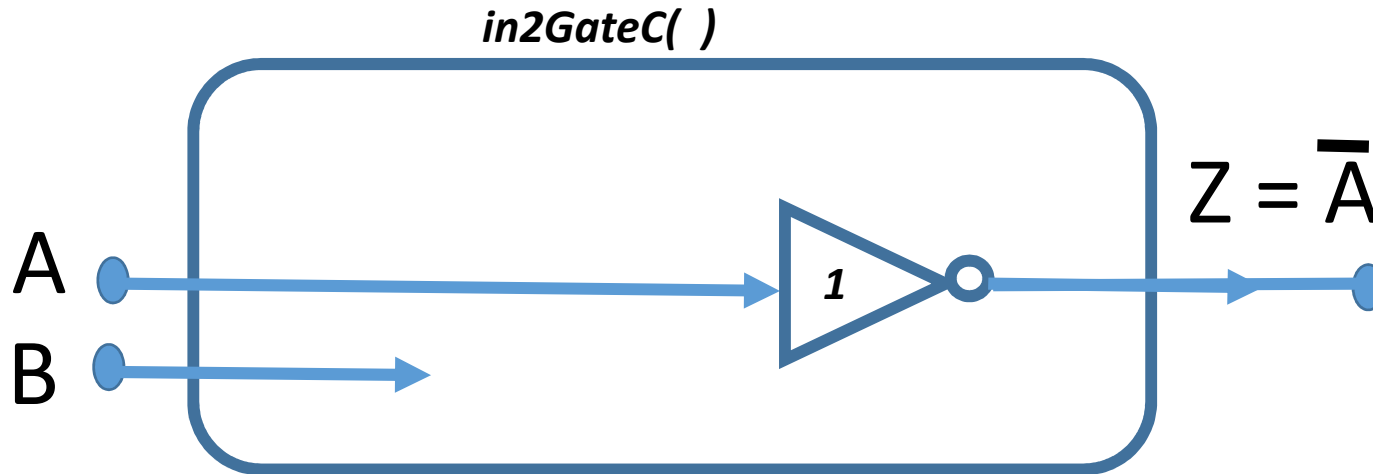

in2GateC() 回路


A	B	Z
0	0	1
0	1	1
1	0	0
1	1	0

DCDL Code for in2GateC() 回路

```
define in2GateC( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = 1 - A ; }
```

$$(12)_{10} = (1010)_2 = (C)_{16}$$

2入力1出力論理ゲート in2GateD()回路の動作説明

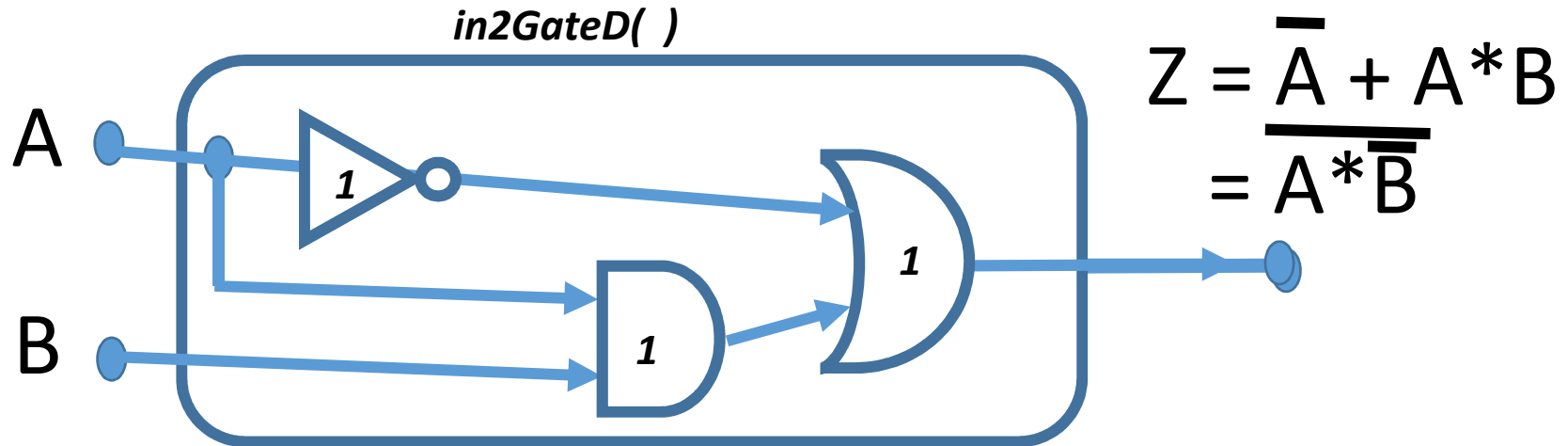

in2GateD() 回路

A	B	Z
0	0	1
0	1	1
1	0	0
1	1	1

DCDL Code for in2GateD() 回路

```
define in2GateD( ) { input A, B ; output Z ;


    memory ZZ ;

    Z = ZZ ;

    ZZ=(1 - A) + A*B ; }
```

$$(13)_{10} = (1101)_2 = (D)_{16}$$

2入力1出力論理ゲート in2GateE()回路の動作説明

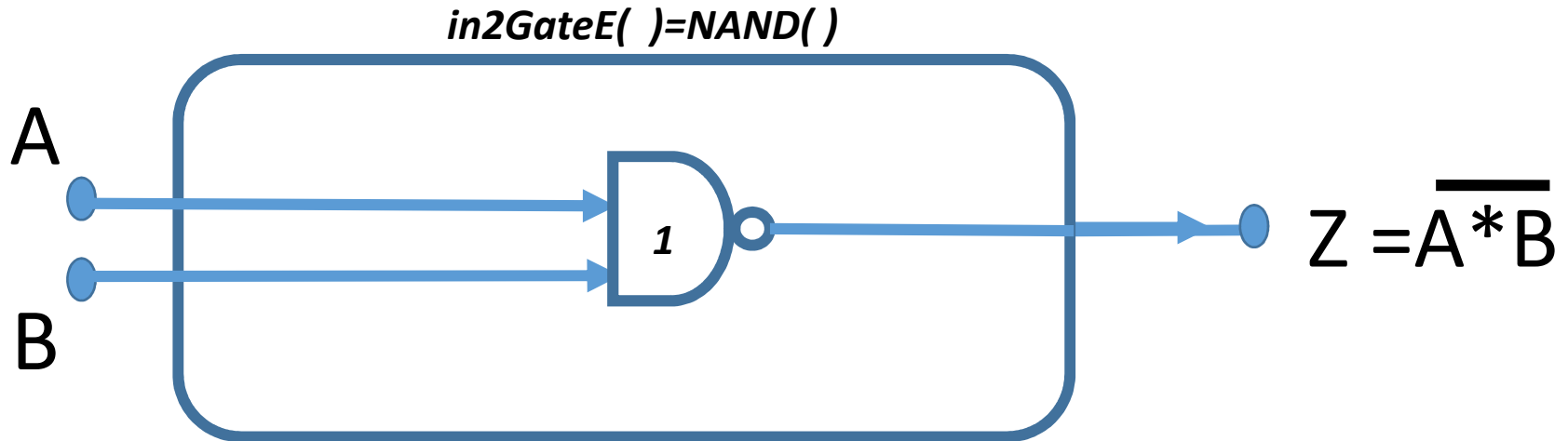

in2GateE() 回路


A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

DCDL Code for *in2GateE()* 回路

```
define in2GateE( ) { input A, B ; output Z ;  
  
    memory ZZ ;  
  
    Z = ZZ ;  
  
    ZZ = (1 - A * B) ; }
```

$$(14)_{10} = (1110)_2 = (E)_{16}$$

2入力1出力論理ゲート *in2GateF()*回路の動作説明

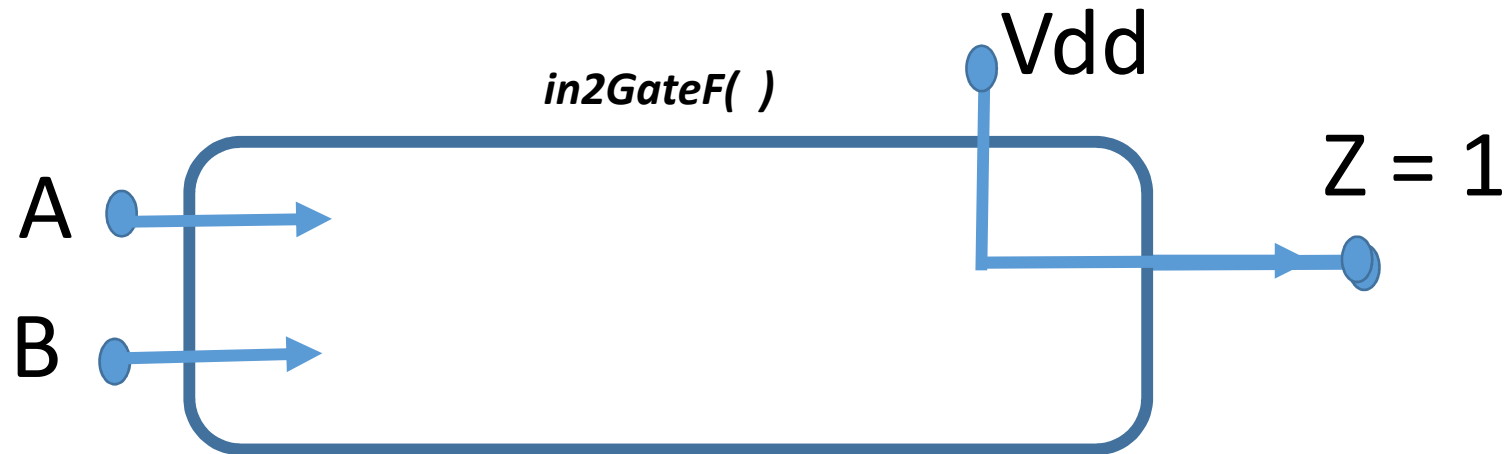

in2GateF() 回路

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	1

DCDL Code for *in2GateF()* 回路

```
define in2GateE( ) { input A, B; output Z;  
                    Z = 1; }
```

$$(15)_{10} = (1111)_2 = (F)_{16}$$

